
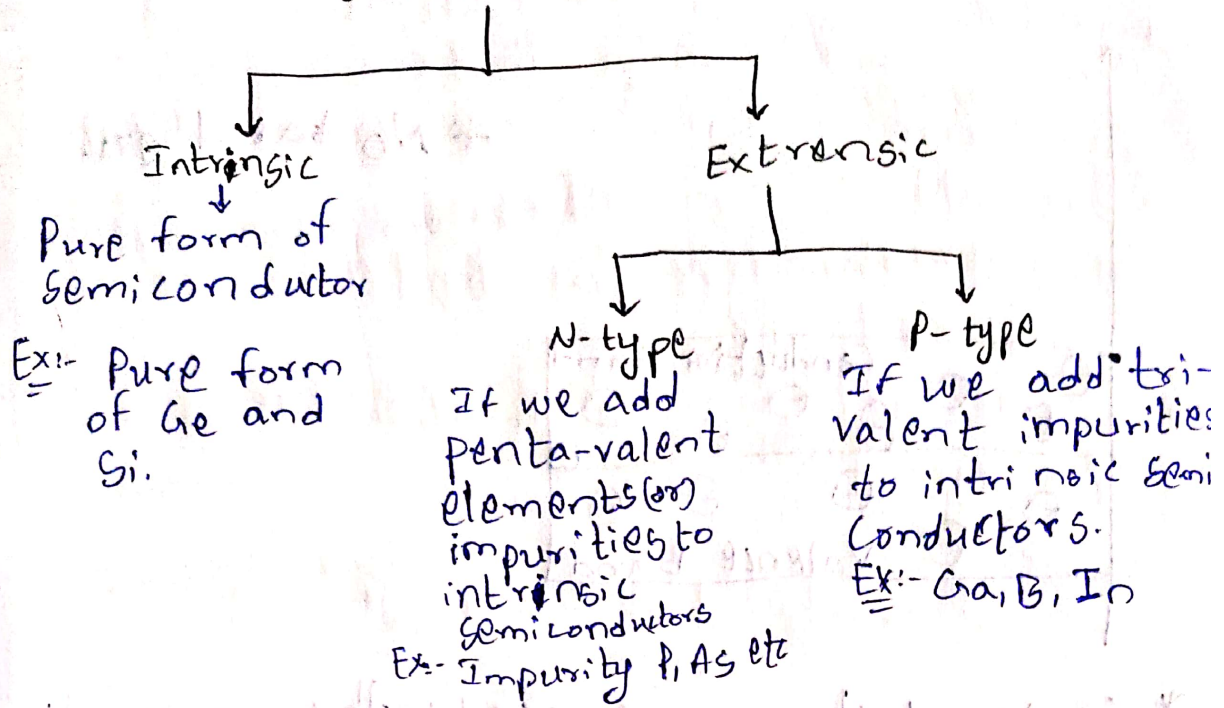



Semiconductor

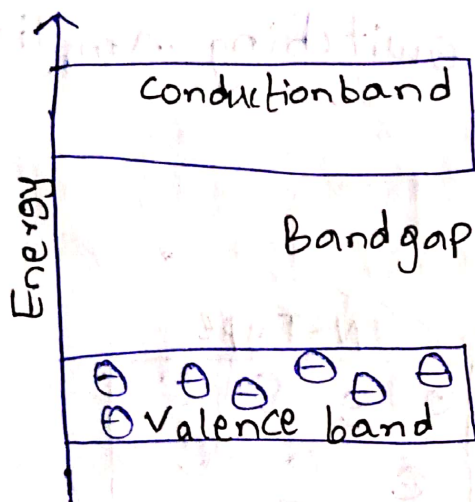


~~Inductor~~
Insulator



Semiconductor

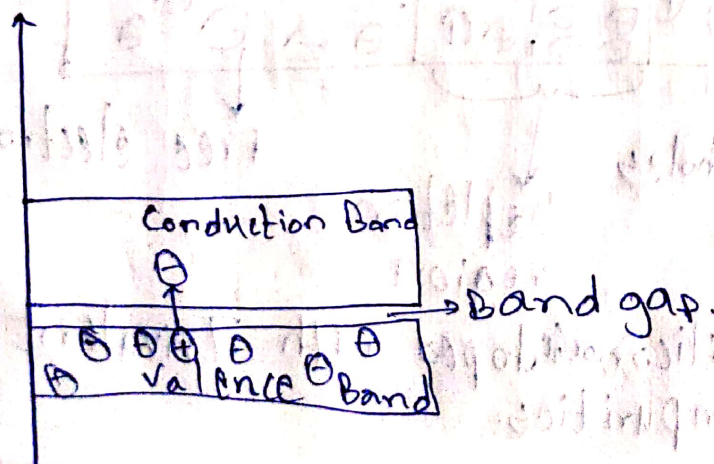


Conductor

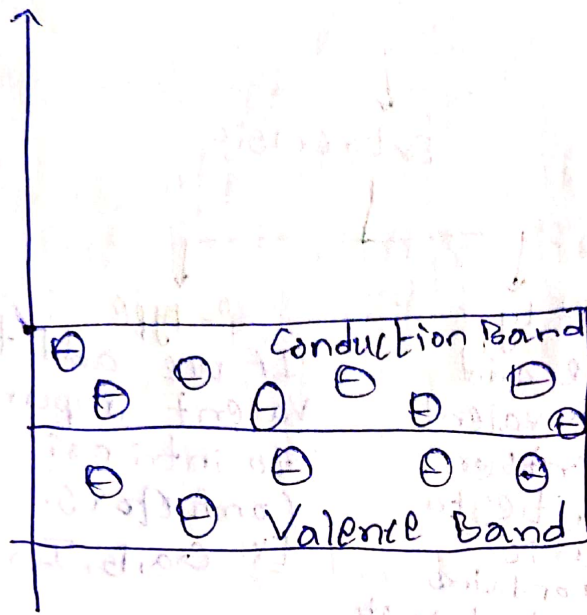

* No band gap

- * Semiconductors are used in the preparation of diodes, transistors & Integrated circuits (IC's).
- * They are used for switching, amplification & signal processing.

PN Junction Diode

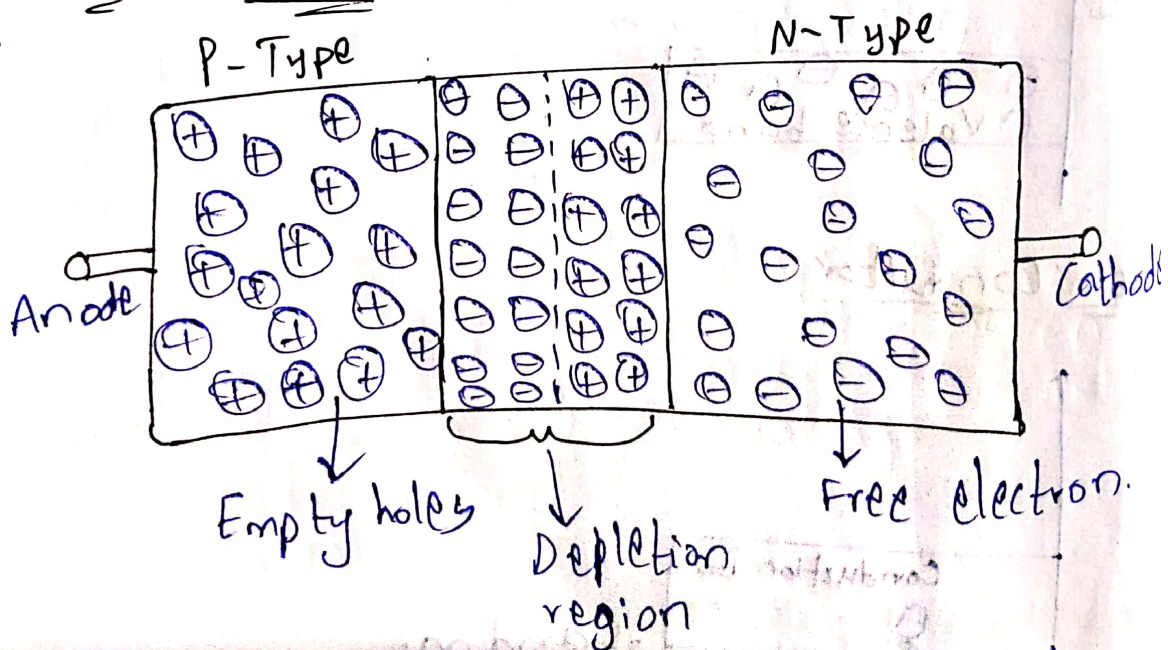


- * P-Type: Silicon doped with Trivalent impurities.


N-Type: Silicon (or) Ge doped with pentavalent impurities.

* A semiconductor diode that allows current flow in only one direction.

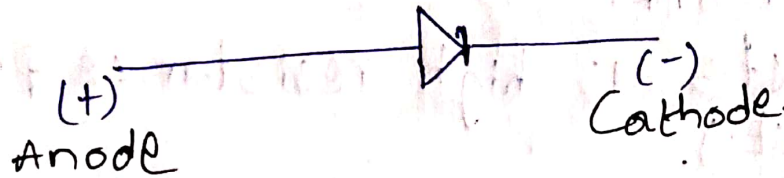* Barrier potential For Silicon = $0.7V$
Germanium = $0.3V$




Forward Bias

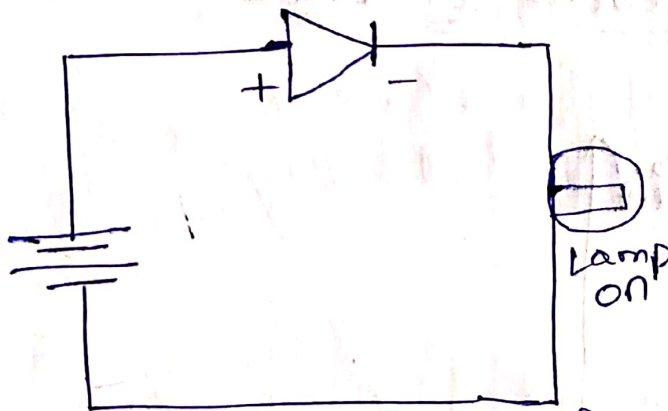

* Here the current is flowing in the conventional direction of current i.e; +ve to -ve so, the current passes through the diode as a result the lamp glows.

* Diode acts as low resistance path. (closed circuit).


Reverse Bias

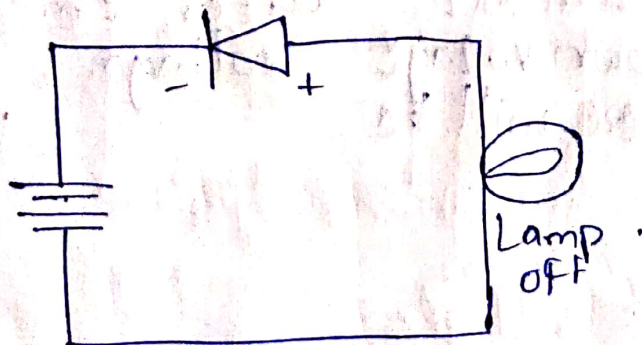

* Here the negative terminal of Diode & positive terminal of Battery is connected & the positive side of diode & negative terminal of battery are connected, as a result there will be no passage of current through the diode so the lamp gets turned off.

* Diode acts as high resistance path (open circuit).

V-I characteristics of Diode

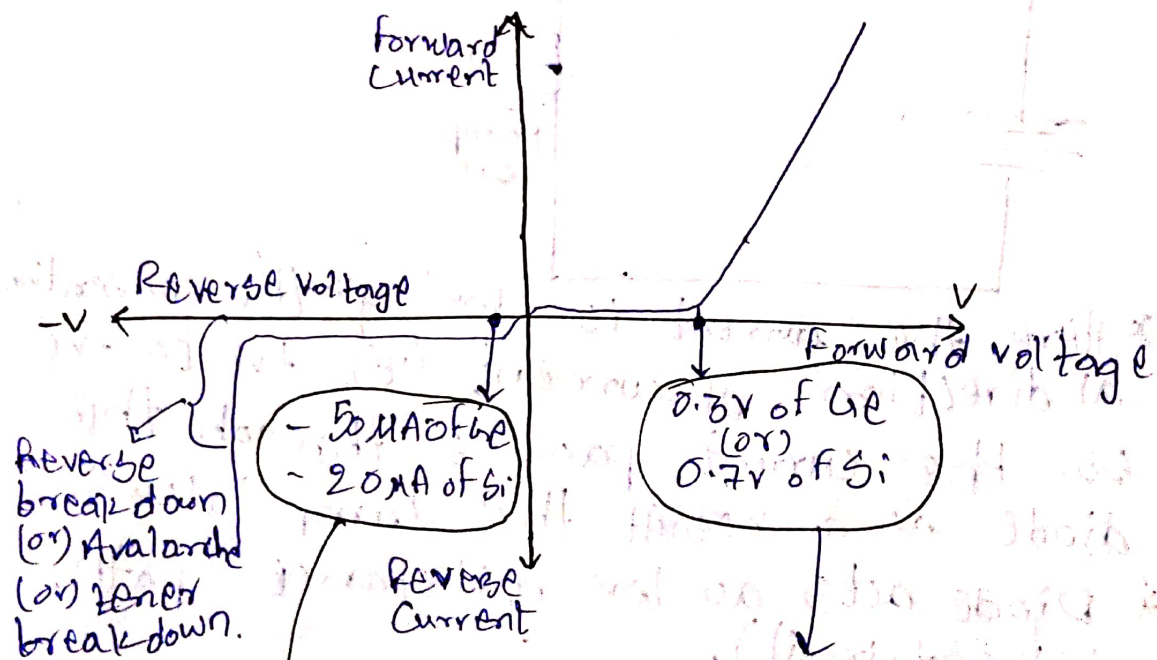

There will be minimal leakage of current until breakdown voltage after that there will be a drastic fall.

Rapid increase in the current after threshold voltage.

Diode Applications

* Diode acts as a switch.

* Rectification :- Converts AC to DC.

Ex:- Full-wave Rectifiers & Half-wave Rectifiers.

* Clipping / Clamping:- Modifies waveform shapes.

* Voltage Regulation: Zener diodes maintain constant voltage.

* Signal mixing / Demodulation: Used in communication circuits.

Diode current Equation

$$I = I_0 \left(e^{\frac{qV}{\eta kT}} - 1 \right)$$

I = Current flowing through the diode.

I_0 = Saturation current.

q = Charge on the electron.

V = Voltage applied across the diode.

η = ideality factor.



k = Boltzmann's constant

$$k = 1.38 \times 10^{-23} \text{ J K}^{-1}$$

T = Temperature in Kelvin.
Absolute.


Rectifier

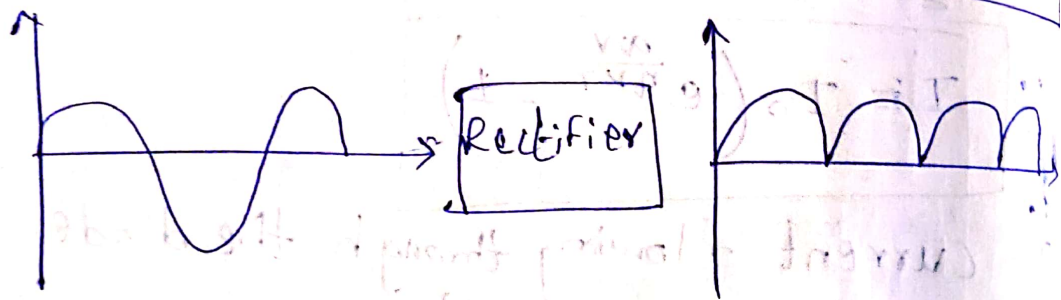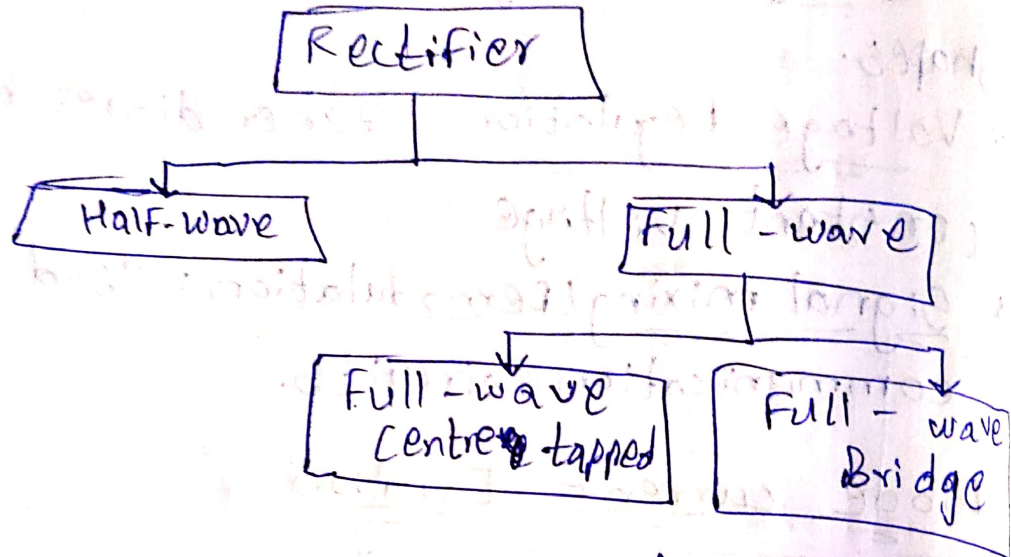- * It is an electronic device that converts AC into DC.
- * It is used in electronic devices where DC power source is required.



- I_{dc}, V_{dc}
- I_{rms}, V_{rms}
- γ = Ripple factor
- P_{dc}, P_{ac} = Output & Input Power.
- f = Form Factor
- η = Efficiency (Ratio of Rectification).
- Regulation.
- Transformer Utilization Factor.
- Peak Inverse Voltage.

Half-Wave Rectifier

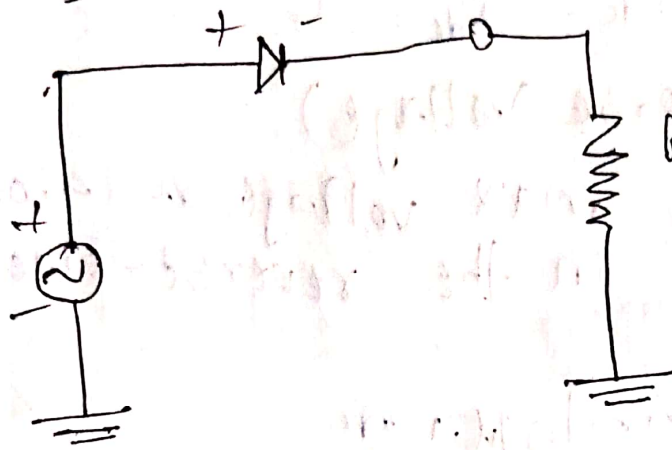

⇒ Reverse Bias
(Diode open circuit).

⇒ Forward Bias
(Diode closed circuit).

$$\rightarrow I_{dc} = \frac{I_m}{\pi}; \quad V_{dc} = \frac{V_m}{\pi}$$

$$\rightarrow I_{rms} = \frac{I_m}{2}$$

$$\rightarrow V_{rms} = \frac{V_m}{2}$$

$$\rightarrow \gamma = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} \Rightarrow \gamma = 1.211$$

* the ripple content in the output are 1.211 times the dc component i.e; 121.1% of the dc component.

$$\rightarrow \eta = \frac{\text{D.C output Power}}{\text{A.C input Power}} = \frac{P_{dc}}{P_{ac}}$$

$$\eta = 40.6\% \text{ (H.W.R.)} = \frac{I_m^2 R_L}{\pi^2}$$

$$\frac{I_m^2}{4} (R_s + R_L + R_D)$$

$$\rightarrow \text{Transformer Utilization Factor} = \frac{I_{dc}^2 R_L}{V_{rms} I_{rms}}$$

* Ratio between the power delivered to the load and the rated ac power from secondary.

$$\boxed{TUF = 0.287}$$

Form Factor = $\frac{I_{rms}}{I_{dc}} = \frac{V_{rms}}{V_{dc}} = 1.57.$

→ PIV (Peak Inverse Voltage)

* This is the max voltage a diode can withstand in the reverse-biased direction.

$PIV = 2V_m \Rightarrow \mu.w.R$

* The only advantage of $\mu.w.R$ is simple circuit & low cost.


* The disadvantages are:-



→ High ripple ~~per~~ content i.e; 121%

→ $\eta = 40.5\%$ which is inefficient.

→ $TUF = 0.287$, the transformer is not fully utilized.

Full wave Center-tapped

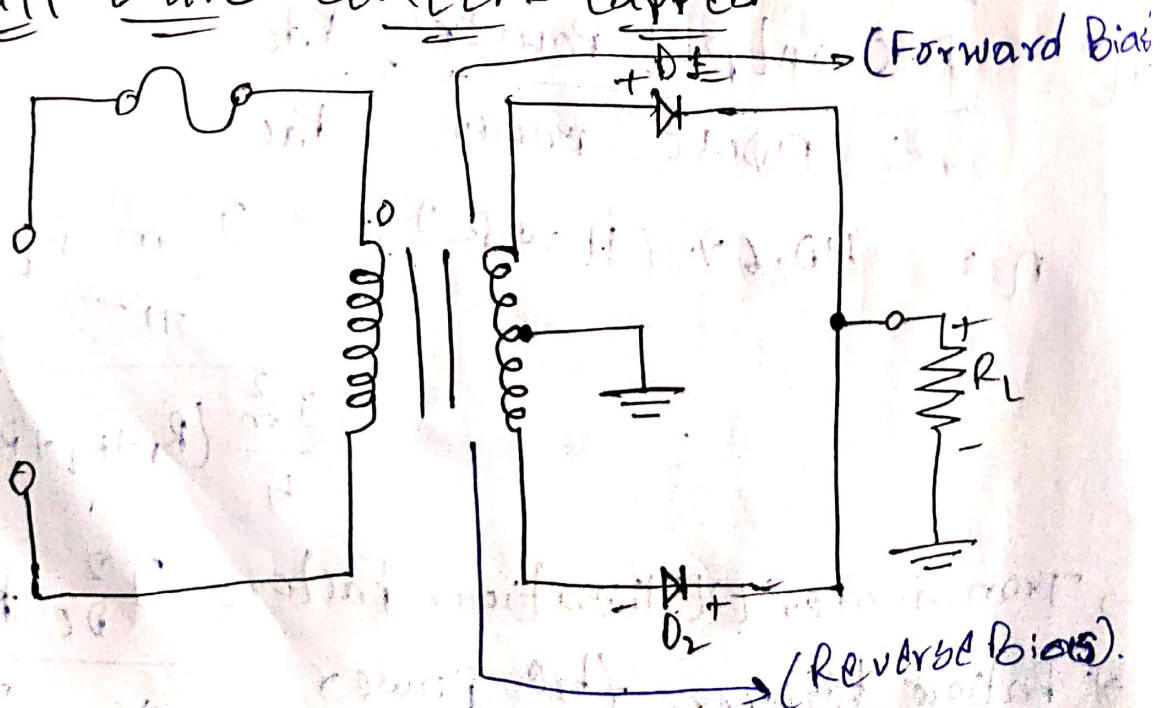

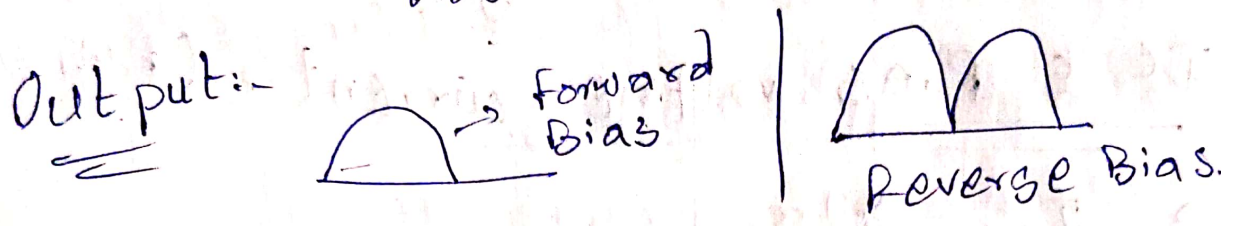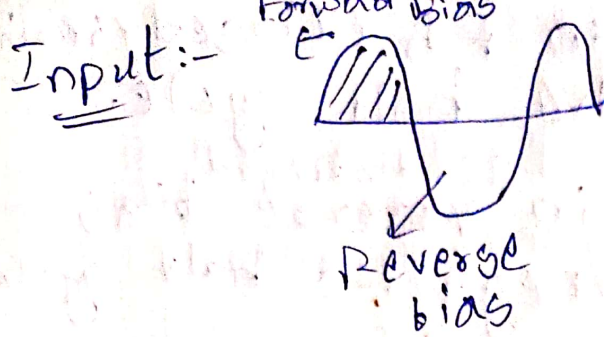


→ If D_1 is closed then it acts as forward bias, else acts as reverse bias.

→ If D_2 is closed then it acts as forward

* If D_1 is ^{in f.B} positive half cycle.
_{it is}

* Else D_2 is F.B it is negative half cycle.

Full wave Bridge Rectifier

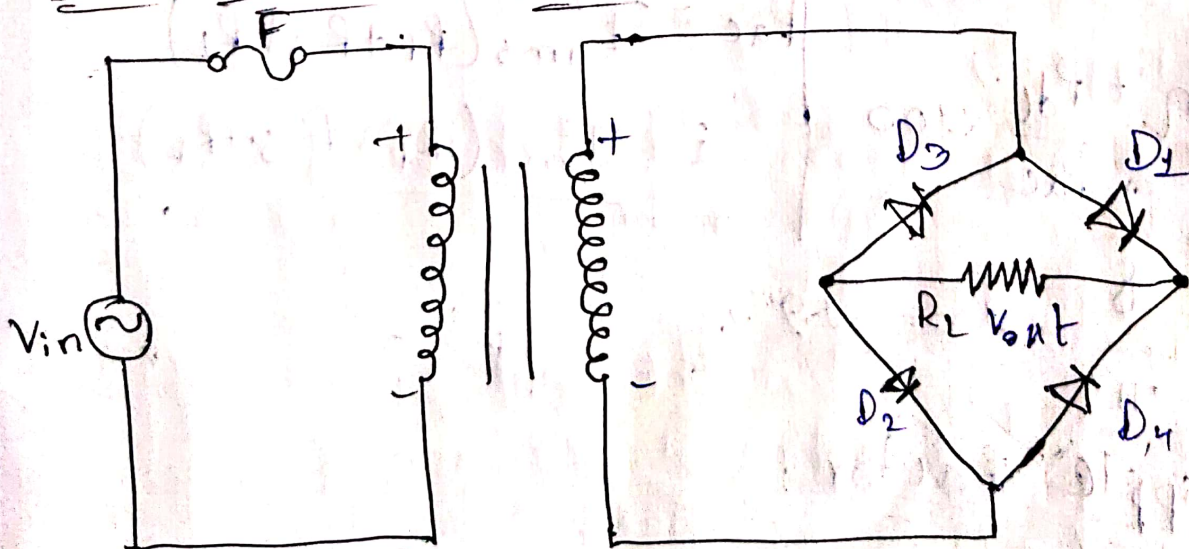

* If D_1 & D_2 are in F.B. (closed circuit) then it is positive half cycle.

* If D_3 & D_4 are in ~~reverse~~^{forward} bias (closed circuit) is negative half cycle.

DC & RMS voltage currents (F.W.R)

$$\rightarrow I_{DC} = \frac{2I_m}{\pi}$$

$$\rightarrow I_{RMS} = \frac{I_m}{\sqrt{2}}$$

$$\rightarrow V_{DC} = \frac{2V_m}{\pi}$$

$$\rightarrow V_{RMS} = \frac{I_m}{\sqrt{2}} R_L$$

* FWR efficiency

$$\eta = \frac{P_{dc}}{P_{ac}}$$

$$\therefore \eta = \frac{P_{dc}}{P_{ac}} \times 100$$

$$= \frac{8}{\pi^2} \times 100 = 81.2\%$$

$$P_{dc} = I_{dc}^2 R_L = \frac{4}{\pi^2} I_m^2 R_L$$

$$P_{ac} = I_{rms}^2 (R_f + R_s + R_L)$$

$$= \frac{I_m^2 (R_f + R_s + R_L)}{2}$$

Ripple factor:

$$\gamma = \sqrt{\left[\frac{I_{RMS}}{I_{DC}}\right]^2 - 1} = \sqrt{\frac{\pi^2}{8} - 1} = 0.48$$

→ TUF:-

$$TUF = \frac{I_{DC}^2 R_L}{V_{rms} I_{rms}}$$


→ PIV:-

$$PIV = V_m$$

Parameters	H.W.R	F.W.R (C.T)	F.W.R (Bridge)
I_{dc}	I_m/π	$2I_m/\pi$	$2I_m/\pi$
V_{dc}	V_m/π	$2V_m/\pi$	$2V_m/\pi$
I_{rms}	$\frac{I_m}{\sqrt{2}}$	$\frac{I_m}{\sqrt{2}}$	$\frac{I_m}{\sqrt{2}}$
V_{rms}	$\frac{V_m}{\sqrt{2}}$	$\frac{V_m}{\sqrt{2}}$	$\frac{V_m}{\sqrt{2}}$
Form Factor	1.57	1.11	1.11
Ripple Factor	1.21	0.48	0.48
P_{dc}	$\left(\frac{I_m}{\pi}\right)^2 R_L$	$\left(\frac{2I_m}{\pi}\right)^2 R_L$	$\left(\frac{2I_m}{\pi}\right)^2 R_L$
P_{ac}	$I_m^2 (R_s + R_f + R_L)/4$	$I_m^2 (R_s + R_f + R_L)/2$	$I_m^2 (R_s + R_f + R_L)/2$
η	40.6%	81.2%	81.2%
PIV	$2V_m$	V_m	V_m
TUF	0.287	$(0.571 + 0.812)/2$	0.812
% Reg	$(R_s + R_f)/R_L$	$(R_s + 2R_f)/R_L$	$(R_s + 2R_f)/R_L$
No. of diodes	2	4	4
frequency	f	$2f$	$2f$

Applications

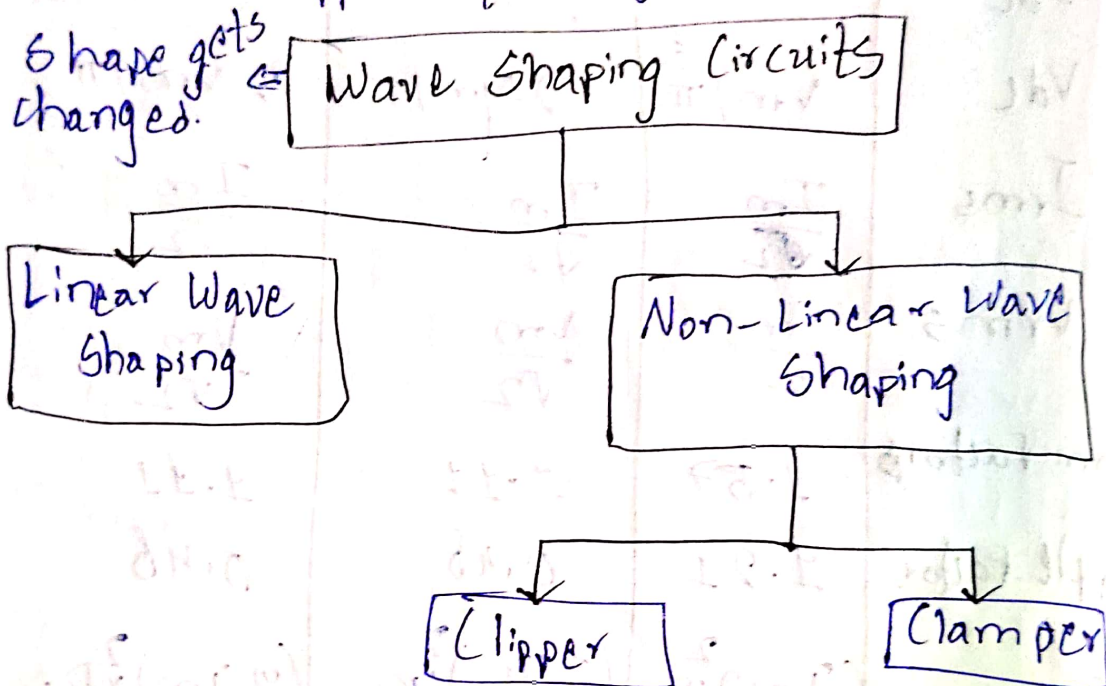- Power supplies, Battery charging
- Signal processing, Electrolysis, Renewable energy systems, Automotive applications.




* Non-linear wave shaping circuits utilize diodes alongside resistors to modify waveforms.

Clippers


* A non-linear wave shaping circuit which can cut or trim the unwanted portion of the waveform.

* It prevents the output waveform from exceeding a certain level, at the same time it does not distort the remaining part of the waveform.


Ex:-

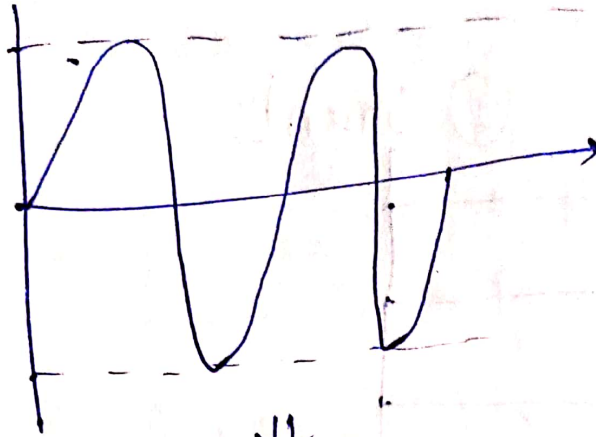

CLIPPER
CIRCUIT

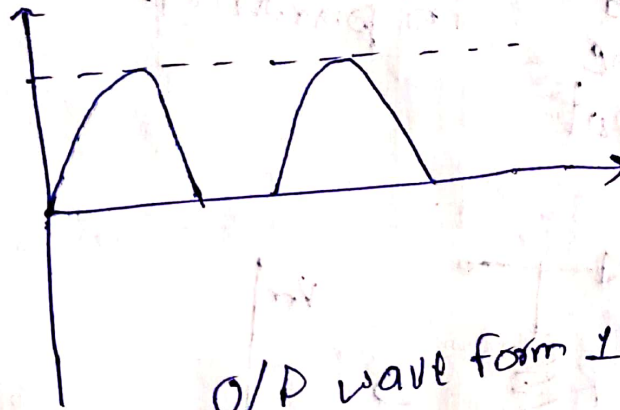


O/P wave form 1

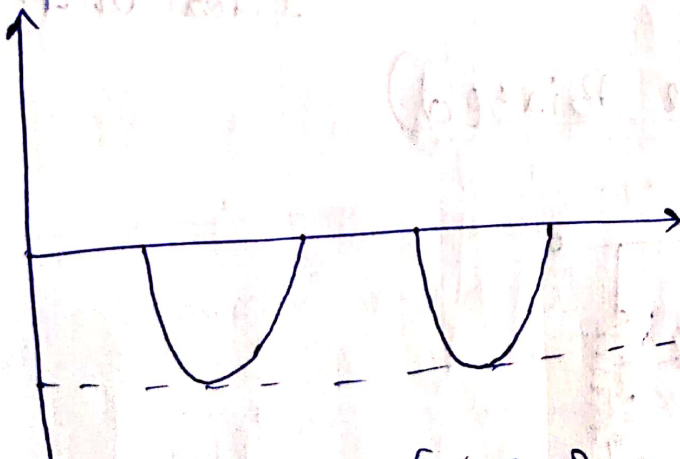



O/P wave form 2

Types

① Series

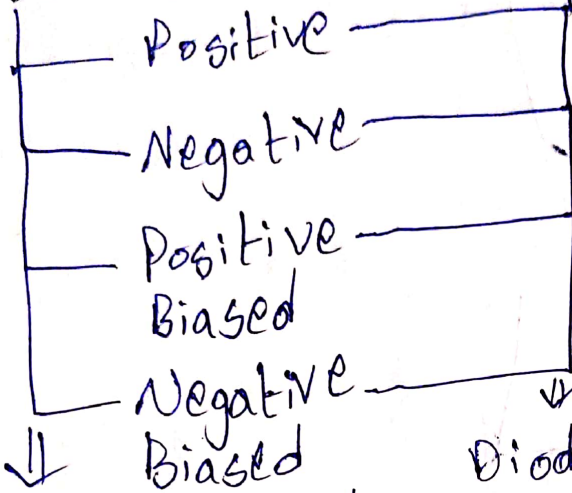


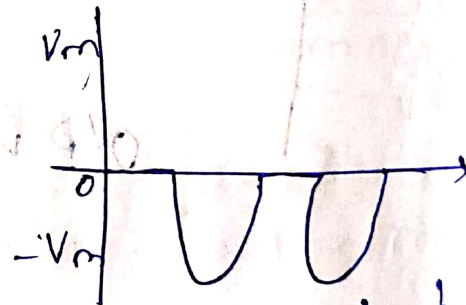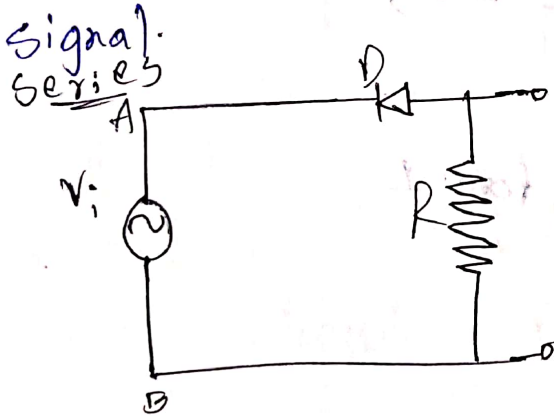Diode is connected in series with the load resistor & input signal.




Ideal output


Series (Positive Biased)

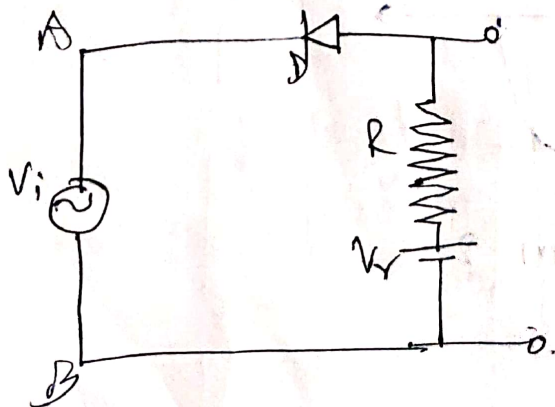


Series (Negative Biased)

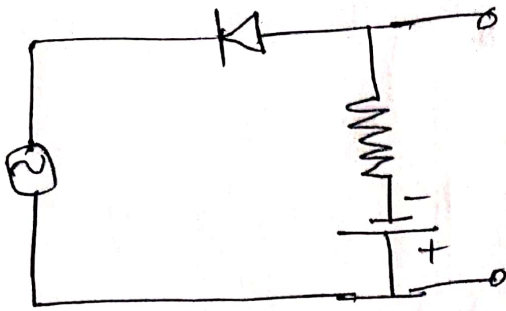


Positive Shunt Clipper

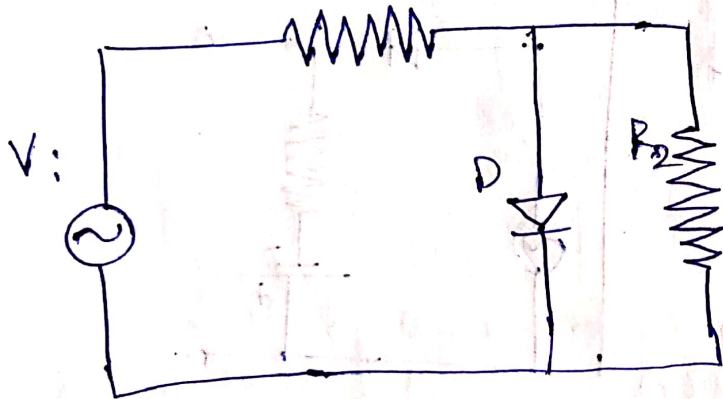


Positive Biased Shunt Clipper

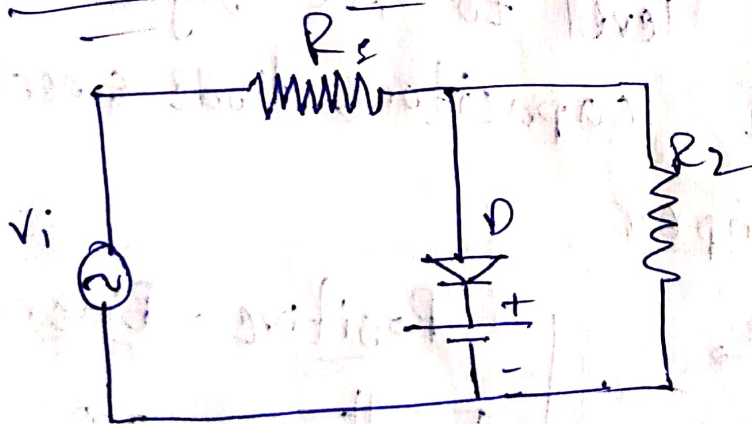


Negative Biased Shunt Clipper

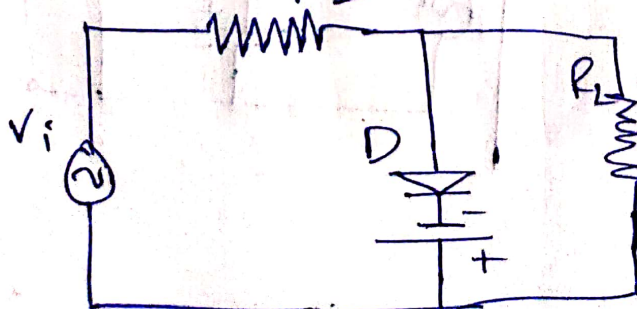


Negative Clipper

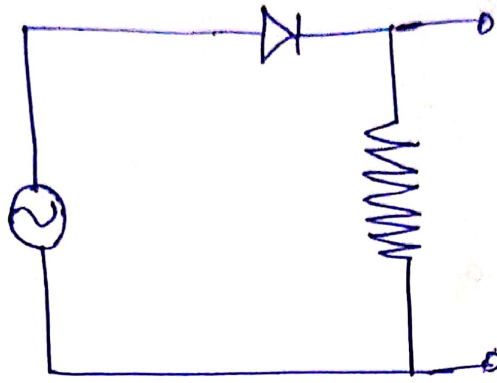

Positive Biased

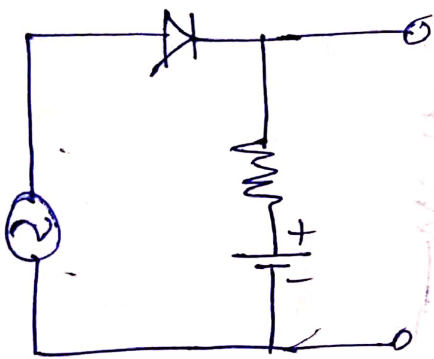

Negative Biased

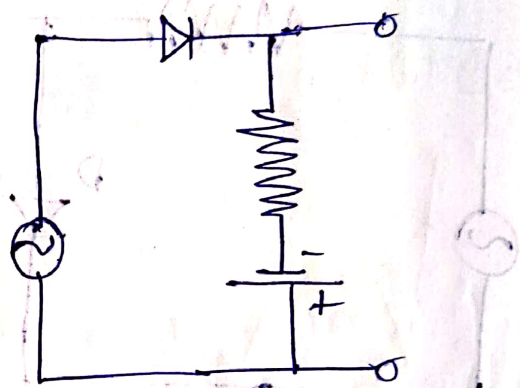


Clamper


→ Adds a DC level to AC signal.

→ They consist capacitors, diode & resistor


Positive clamper

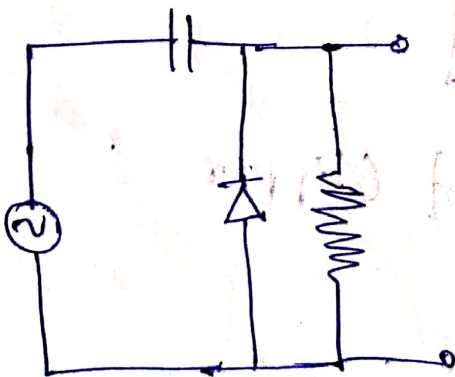


Positive - Biased

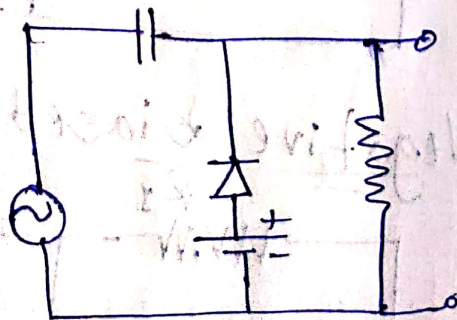


Negative - Biased

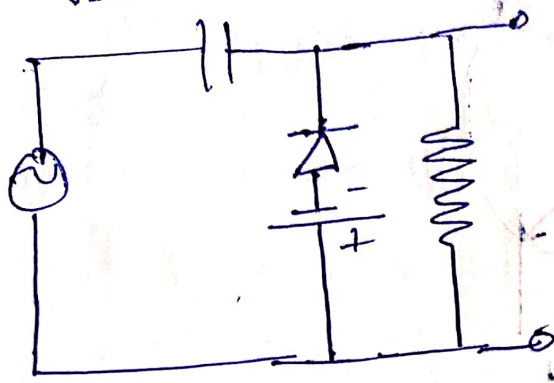


Negative Clamper

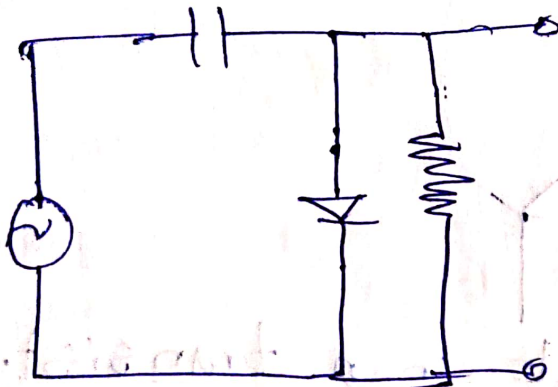

Positive - Biased

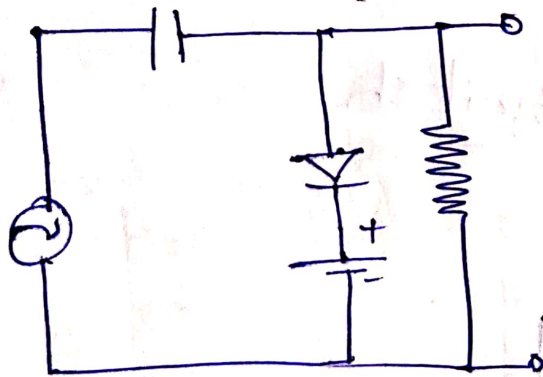


(Negative - Biased)

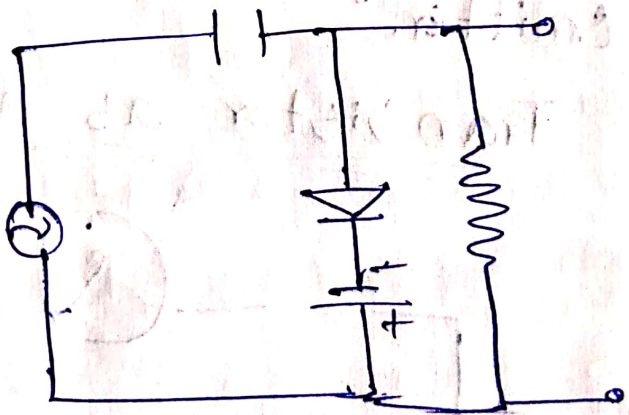


Transistor

NPN →

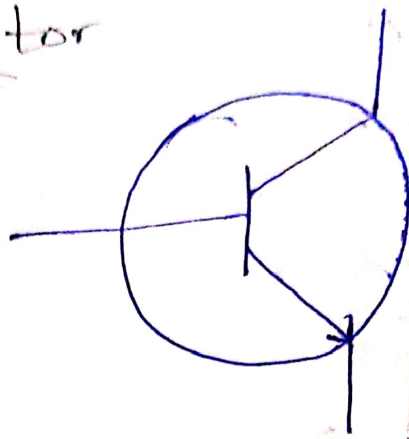



PNP →

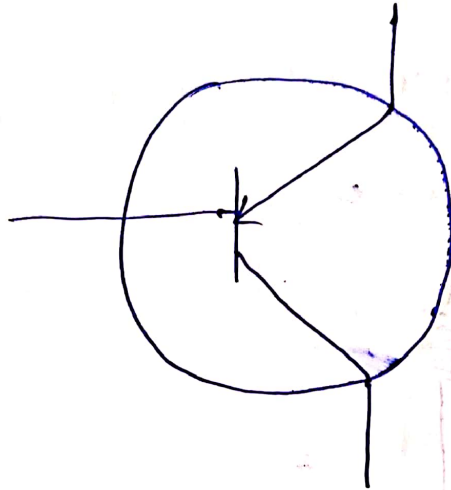

* Controlled current in a transistor should go between the collector & the emitter.

Transistor as a switch

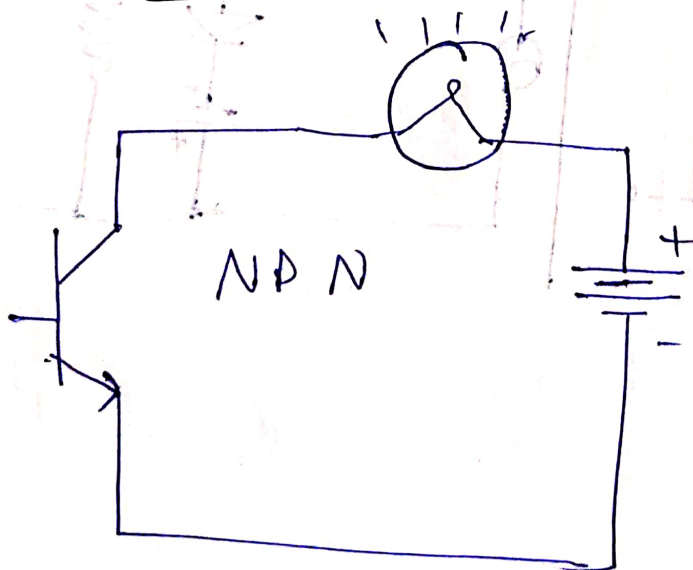

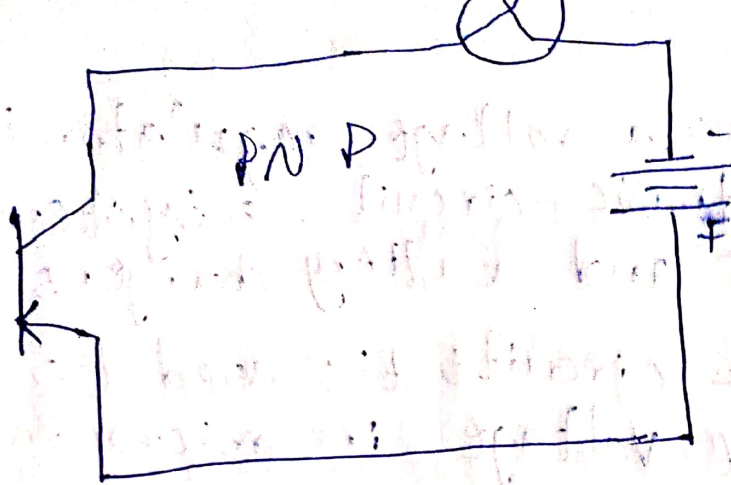


* When a transistor has maximum current through it, it is said to be in a state of saturation. (Fully conducting).

* When a transistor has zero current through it, it is in a state of cutoff (non-conducting).

Zener Diode

→ It is a semiconductor device that allows current to flow in the reverse direction when a certain voltage is applied, effectively acting as voltage regulator.

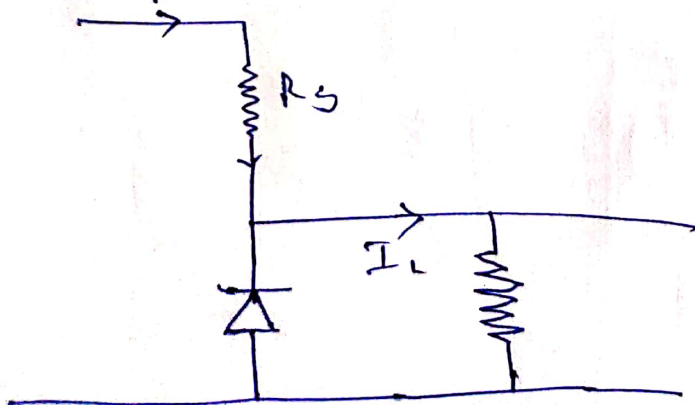→ When voltage exceeds breakdown voltage diode begins to conduct & regulate the voltage.



⇒ Zener diode acts as voltage regulator.

Applications

* Zener diode as a voltage regulator is used in electronic circuit & system power supplies and battery chargers.

* In electronic circuits it is used to regulate the voltage in microcontrollers, sensors, amplifiers, etc.

CO-4 INTEGRATED CIRCUIT

- In an IC millions of resistors, transistors & capacitors are fabricated.
- Multiple electronic components are fabricated on a single chip of semiconductor material then it is an IC.

Advantages

- Compact size
- Lesser weight
- Low power consumption
- Reduced cost
- Increased reliability.
- Better operating speeds.

Types

① Analog Integrated Circuits

- IC's that operate over an entire range of continuous values of signal amplitude are called as Analog IC's.

Ex:- Op-amps, voltage regulators & audio amplifiers.

② Digital IC's

- IC's that process discrete signals or information represented as a sequence of numbers.

Ex: microprocessors, memory chips & logic gates.

Characteristics of Analog IC's

- ① Continuous Signal Processing.
- ② Signal Accuracy & Precision.
- ③ Variable Voltage levels
- ④ Complexity & Precision in Design.
- ⑤ Low Power Consumption.

Characteristics of Digital IC's

- ① Binary Signal Processing
- ② Boolean logic operations.
- ③ Robustness to Noise
- ④ Design Scalability.
- ⑤ Power Consumption.
- ⑥ Data storage & Processing.

* Analog IC's consist less number of transistors compared to digital IC's

Voltage Regulators
* Voltage Regulator is an electronic device that maintains a constant output voltage level.

* It ensures a stable & reliable power supply for electronic devices.

* As the variation in voltage in electronic devices leads to malfunctions. So, we use voltage regulators.

Types (According to working Principle).

① Linear Voltage Regulators

→ Uses a series pass transistor to adjust the output voltage.

→ Limited efficiency.

② Switching Voltage Regulators

→ These regulators switch the input voltage ON & OFF rapidly & use inductors & capacitors to filter the output.

→ Provide higher efficiency.

→ According to voltage generated.

③ Positive Voltage Regulators

* Positive voltage.


Ex:- LM 78XX series.

② Negative V.R

* Negative voltage

Ex:- LM 79xx.

LM 7805

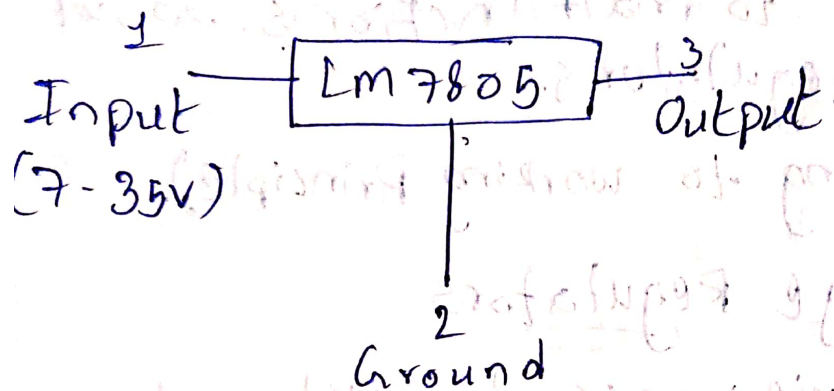

* Max efficiency for an input is 7.2V


* Fixed positive output voltage is 5V.

* Other variants include LM7805, LM7805C, LM7805CT which can handle upto 1A.

Applications

- Current regulator.
- Regulated dual supply.
- Building circuits for Phone Charger, UPS, power supply circuits, portable CD Player.
- Adjustable output regulator.
- Fixed output regulator.

LM 7905

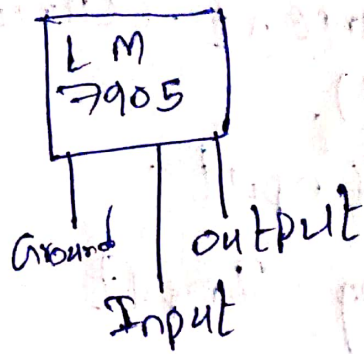

* Receives the regulated output of -5V.

* Input voltage range is -7V to -25V.


* Other variants include LM 7905, LM 7905, LM 7905 CT, up to $\pm 1A$.

Applications


- Used for op-amp signals.
- Regulated Dual Supply.
- Limits current in certain applications.

LM 723

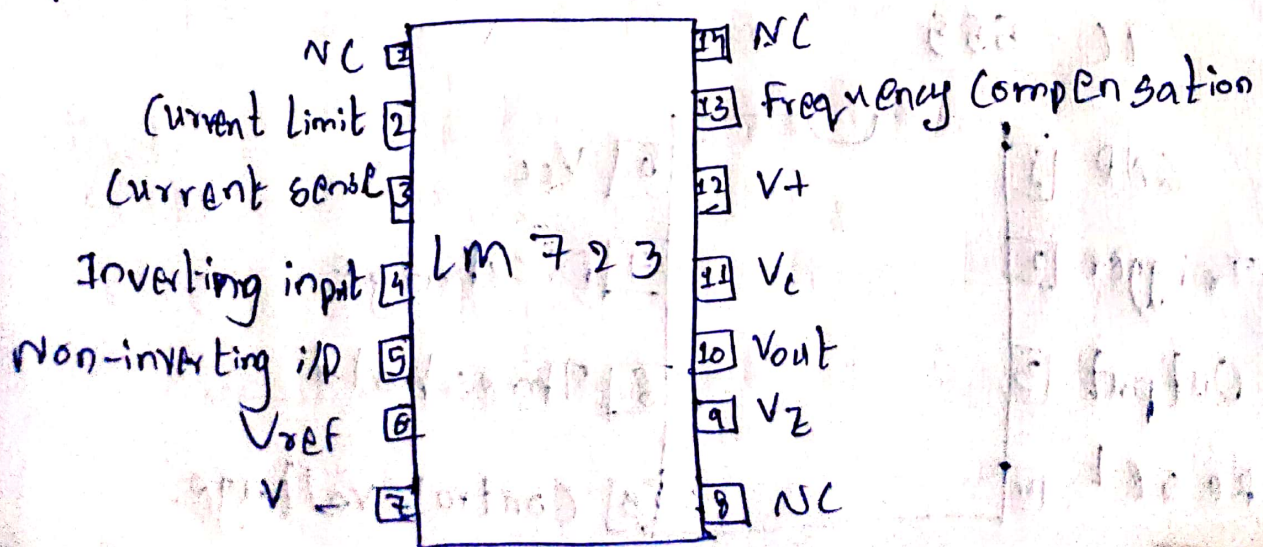→ It is a changeable voltage regulator used in the series regulator application with 50mA current output without exterior pass transistor.



- Pin 1 :- Not Connected.
- Pin 2 :- Limits the current. (Current)
- Pin 3 :- (Current Sense).
- Pin 4 :- Inverting Input.
- Pin 5 :- Non-Inverting Input.
- Pin 6 :- provides 7V reference voltage.
- Pin 7 :- GND
- Pin 8 :- NC
- Pin 9 :- This pin used to make negative regulators.
- Pin 10 :- DIP pin.
- Pin 11 :- This is series pass transistor collector input.
- Pin 12 :- Positive supply.
- Pin 13 :- Decreases noise with a 100 pF capacitor.
- Pin 14 :- NC



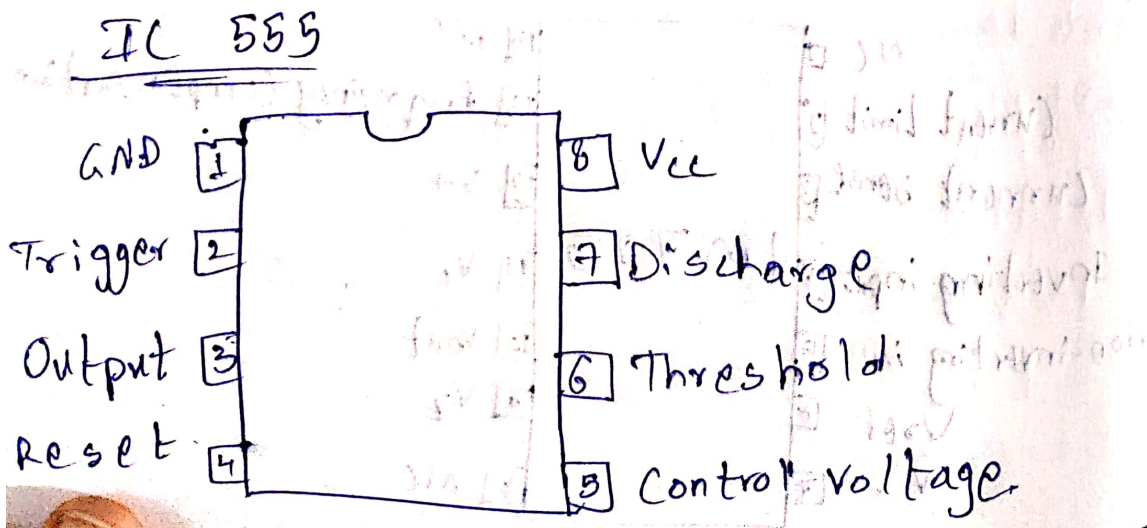


Applications

- Timers
- Dimmer circuits
- PULSE generator circuits.
- Square wave generators.
- Duty cycle adjuster.

Operational Amplifier

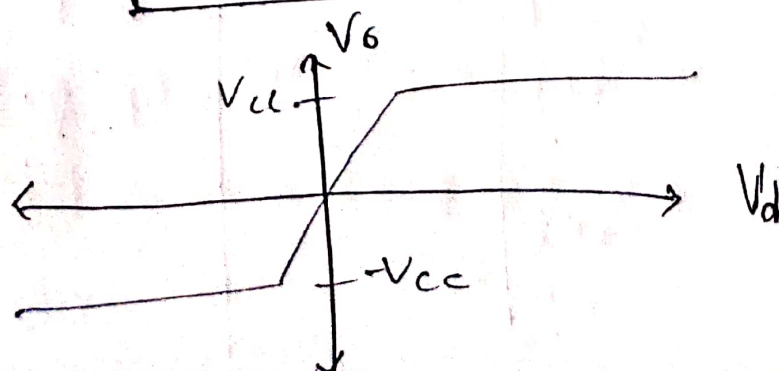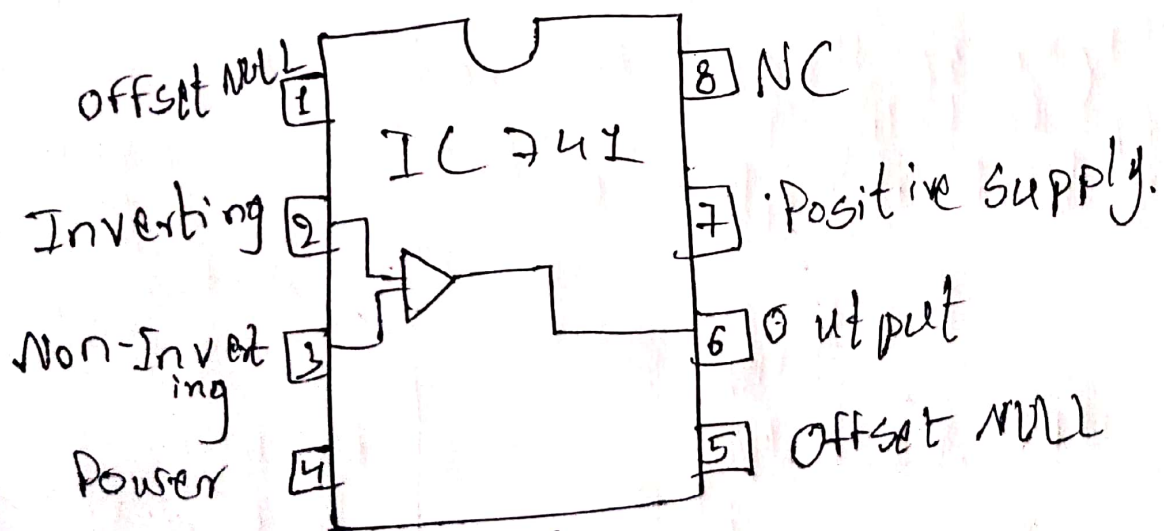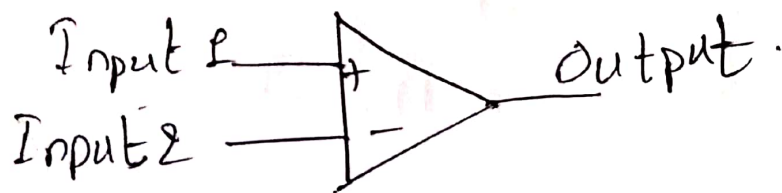- Op amp performs mathematical operations by using analog signals.
- Used to build many analog circuits, filters, oscillators, amplifiers.



Applications

- Voltage follower
- Inverting amplifier
- Non-inverting amplifier
- Summing amplifier
- Differential amplifier
- Integrator